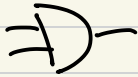


CS 315-02 Combinational Logic

AND




OR




NOT




Circuit

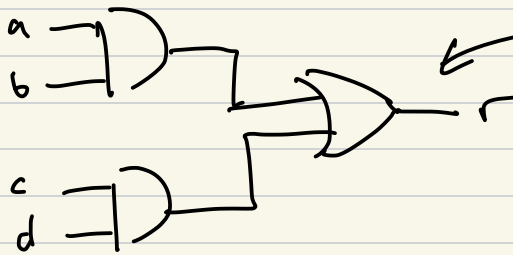

Combinational Logic

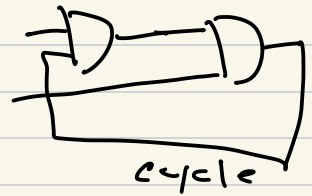

Goal

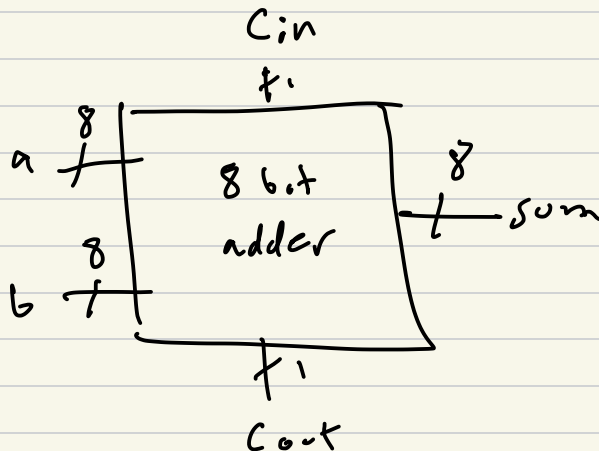

sum-of-products

function:

input: a 3bit number (3 bits)
 $n_2 \ n_1 \ n_0$

output: two bits: even, odd

goal: determine if the number of "1" bits are even or odd

$n_2 \ n_1 \ n_0$

0 1 0 $\rightarrow$ odd
 1 1 0 $\rightarrow$ even

sum-of-products

- 1) truth table
- 2) identify row with "1" output
- 3) build the sop equation

n_2	n_1	n_0	even	odd
✓	0	0	0	1
	0	0	1	0
	0	1	0	1
✓	0	1	1	0
	1	0	0	1
	1	0	1	0
	1	1	0	1
	1	1	1	0

product terms

$$\text{even} = (\bar{n}_2 \cdot \bar{n}_1 \cdot \bar{n}_0) + (\bar{n}_2 \cdot n_1 \cdot n_0)$$


sum term

$$+ (n_2 \cdot \bar{n}_1 \cdot n_0) + (n_2 \cdot n_1 \cdot \bar{n}_0)$$


$$\text{odd} = \overline{\text{even}}$$

$$(\overline{0} \cdot \overline{0} \cdot \overline{0})$$

$$(1 \cdot 1 \cdot 1) = 1$$

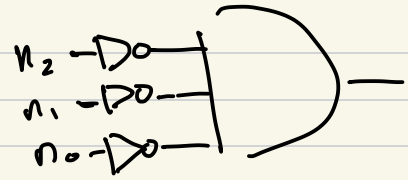

n_2 n_1 n_0

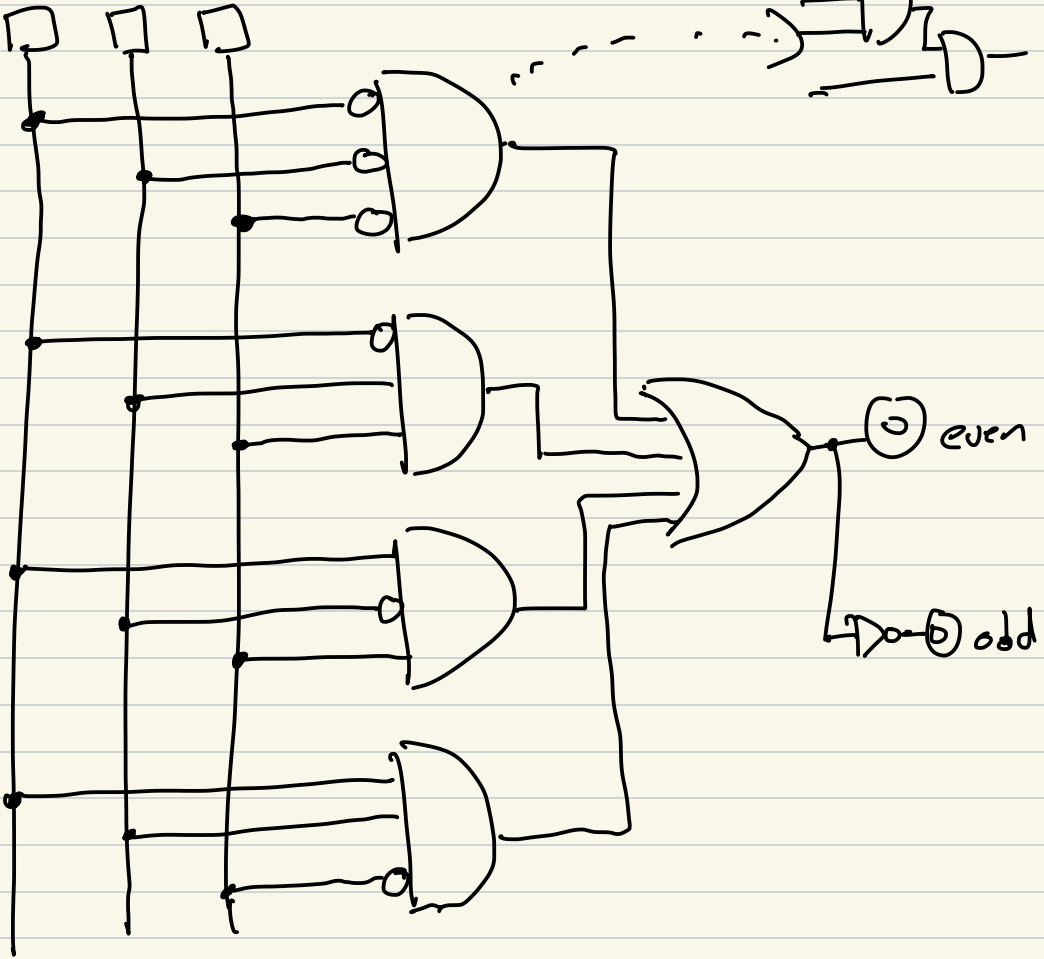

Lab 08 part 2

max2 finds the max value of two 2-bit numbers

$$a = 01$$

$$b = 10$$

$$\text{max2}(a, b) = 10$$

$$\text{max2}(01, 10) = 10$$

$2^{4,16}$

$a_1, a_0 \quad b_1, b_0$				r_1, r_0
0	1	1	0	


SOP

$$f_1 = \underline{\quad + \quad + \quad}$$


$$r_0 = \underline{\quad + \quad + \quad}$$

Goal: Implement an 8-bit Adder

1-bit adder

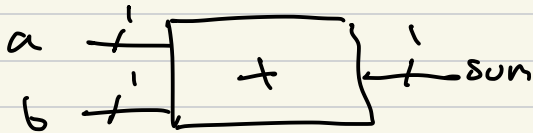

1-bit half adder

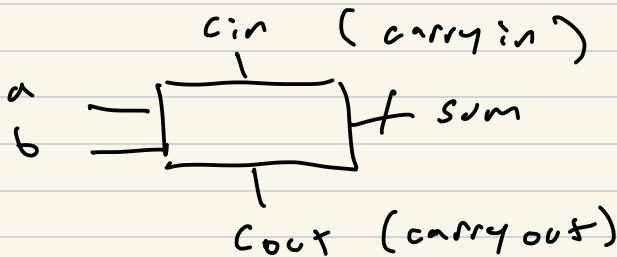

1-bit full adder


grade school
arithmetic

$$\begin{array}{r} \boxed{0} \boxed{0} 1 \\ + 0 1 1 \\ \hline 0 0 \end{array}$$

$$\begin{array}{r} \boxed{0} 1 0 1 \quad \boxed{?} \leftarrow \\ + 0 1 1 0 \\ \hline \end{array}$$

a	b	cin	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

8 bit adder

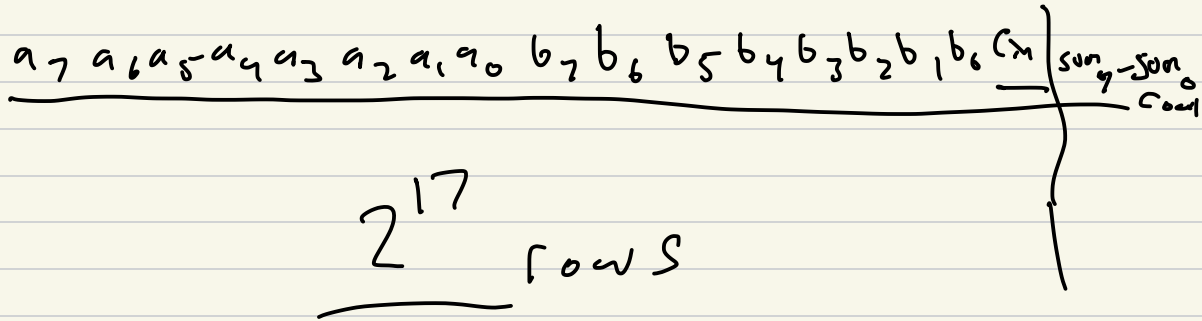

Combine 8, 1-bit full adder,
to build an 8-bit ripple-carry adder

