 


CS 315-02 Processor Decoding 2025-10-30

Lab 09 testing

PC



255

254

1

0


word
4 bytes


Memory

addr_byte


$$\text{addr_word} = \text{addr_byte} / 4$$
 
$$\text{addr_word} = \text{addr_byte} \gg 2$$




 

(1)


 


(2)

 


*

(3)

  

Shift amt 2 bits

 



0
1
2
3
4

Shift and 3 bits




4 bits

2^7


 


 


Reg Decoder

 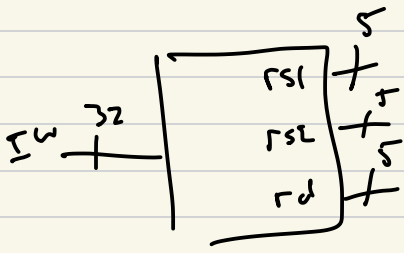 


Immediate Decoder

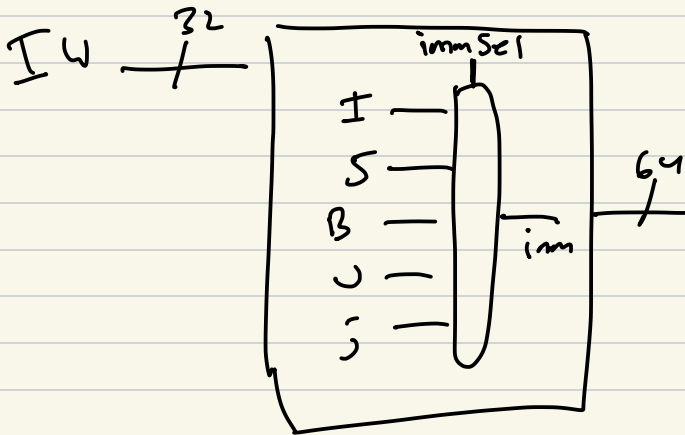 

S-Type Immediate

 

Goal: construct a 64 bit signal value

 

How to implement the sign extender

