

Project 07 Q & A

Advanced Architecture

Final Exam Practice Problems

---

Speculative Execution

Out of order Execution


ld  $t_0$ , (a0)

add  $t_1$ ,  $t_2$ ,  $t_3$

# Question 1

	a	b	c	maj
	0	0	0	0
	0	0	1	0
	0	1	0	0
J	0	1	1	1
	1	0	0	0
✓	1	0	1	1
	1	1	0	1
	1	1	1	1
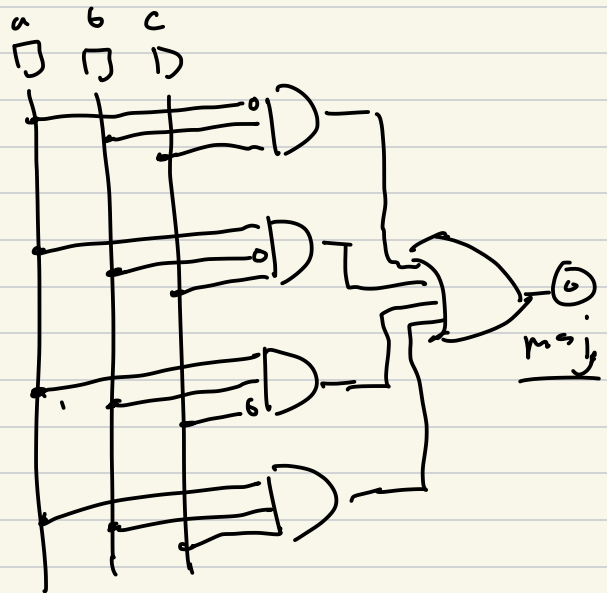
$$\text{maj} = (\bar{a} \cdot b \cdot c) + (a \cdot \bar{b} \cdot c) + (a \cdot b \cdot \bar{c}) + (a \cdot b \cdot c)$$



# Question 3

